
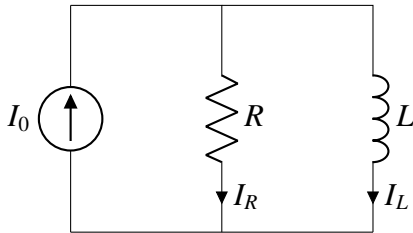


# NCERT Question 11.9.3.9

EE23BTECH11019 - Faisal Imtiyaz \*

**Question:** The R-L circuit with  $R = 10k\Omega$  and  $L = 1mH$  is excited by a step current  $I_0 u(t)$ . At  $t = 0^-$ , there is a current  $I_L = I_0/5$  flowing through the inductor. The minimum time taken for the current through the inductor to reach 99% of its final value is ...  $\mu s$  (rounded off to two decimal places).

**Solution:**

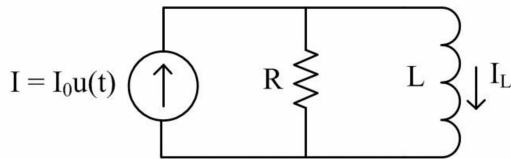

Transform	Signal
$\frac{1}{s(s+a)}$	$\frac{1}{a}(1 - e^{-at})$
$\frac{1}{s+a}$	$e^{-at}$

TABLE 1

INVERSE LAPLACE TRANSFORM PAIRS

$$I_0 u(t) = I_R + I_L \quad (1)$$

From KVL, we have:

$$I_R(R) - L \frac{dI_L}{dt} = 0 \quad (2)$$

$$(I_0 u(t) - I_L)(R) - L \frac{dI_L}{dt} = 0 \quad (3)$$

$$\left(\frac{I_0}{s} - I(s)\right)R - L(sI(s) - I_L(0^-)) = 0 \quad (4)$$

After Simplyfying we have:

$$I(s) = \frac{I_0 R + L s I(0^-)}{s(R + L s)} \quad (5)$$

$$I(s) = \frac{I_0 R}{L} \frac{1}{s(s + \frac{R}{L})} + \frac{I_0}{5} \frac{1}{\frac{R}{L} + s} \quad (6)$$

From Table 1, we have:

$$I(t) = \frac{I_0 R}{L} \left[ \frac{1}{\frac{R}{L}} (1 - e^{-\frac{R}{L}t}) \right] + \frac{I_0}{5} e^{-\frac{R}{L}t} \quad (7)$$

$$I(t) = I_0 - \frac{4}{5} I_0 e^{-\frac{R}{L}t} \quad (8)$$

$$I(t) = I_0 - \frac{4}{5} I_0 e^{-10^7 t} \quad (9)$$

$$\lim_{t \rightarrow \infty} I(t) = I_0 \quad (10)$$

Now time when current in inductor is 99% of its final value is given by:

$$0.99 I_0 = I_0 - \frac{4}{5} I_0 e^{-\frac{R}{L}t} \quad (11)$$

$$0.01 I_0 = \frac{4}{5} I_0 e^{-\frac{R}{L}t} \quad (12)$$

$$t = \frac{L}{R} \ln(80) \quad (13)$$

$$t = 10^{-7} \ln(80) \mu s \quad (14)$$

$$t = 0.43 \mu s \quad (15)$$

